

DDCO Mini Project ISA Submission


Project Title: 8-bit Prefix Adder

Section : E



Batch Details

Student Name	SRN
PARIMALA S	PES1UG19CS323
PARIMALA V	PES1UG19CS324
PAVAN KARTHICK M	PES1UG19CS325
PAVAN KUMAR	PES1UG19CS326

Circuit Diagram:

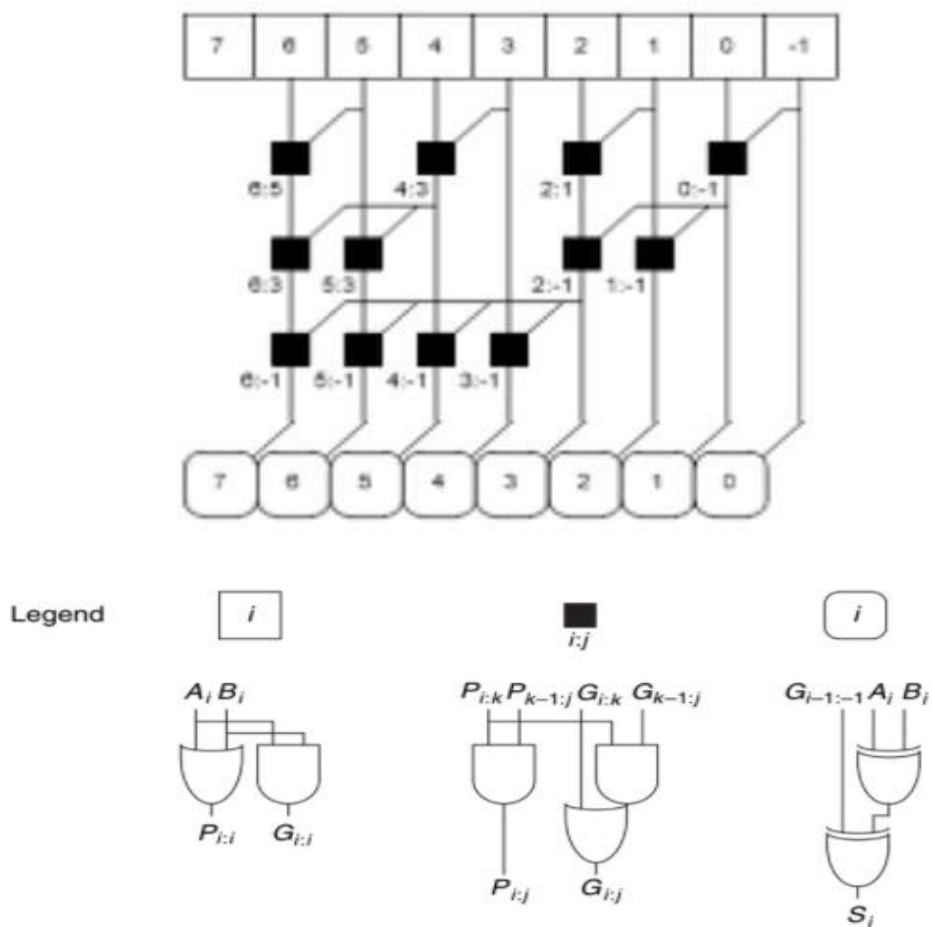

HAND-DRAWN DIAGRAM:

 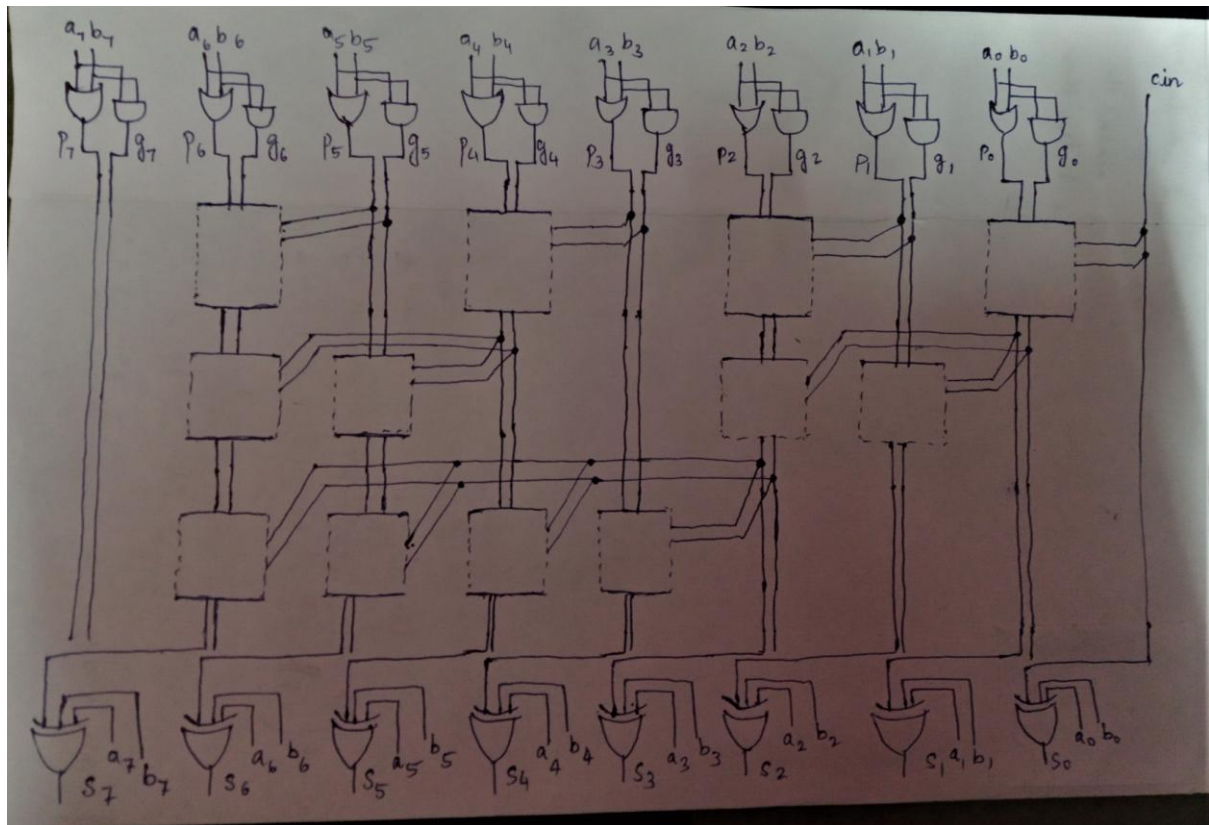

Algorithm (if any):

1. Start

(Create modules for basic operations such as 2-input, or – 2-input , xor gates -2,3 input.)

2. Take 2 inputs a, b each 8 bit size. Initialize a third input cin to 0.
3. Compute the propagate and generate values for all the 8 bits using

$$P_i = a_i + b_i$$

$$G_i = a_i * b_i$$

4. Computation of Carry Generation for each bit: using the formula

$$P_k = P_i * P_j$$

$$G_k = G_i + (G_j * P_i)$$

In general:

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$

$$P_{i:j} = P_{i:k} P_{k-1:j}$$

5. Generate the sum bit for each bit of Inputs and output the sum – 8bits.

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

6. Stop.

Implementation (Code):

MAIN CODE – IMPLEMENTATION FILE:

prefix_add.v:

```
//prefix adder 8 bits
```

```
module and2 (input wire i0, i1, output wire o);
```

```
    assign o = i0 & i1;
```

```
endmodule
```

```
module or2 (input wire i0, i1, output wire o);
```

```

        assign o = i0 | i1;
endmodule

module xor2 (input wire i0, i1, output wire o);
    assign o = i0 ^ i1;
endmodule

module xor3 (input wire i0, i1, i2, output wire o);
    wire temp;
    xor2 xor2_0 (i0, i1, temp);
    xor2 xor2_1 (i2, temp, o);
endmodule

module prop_gen(input wire x,y, output wire p,g);
    or2 o(x,y,p);
    and2 a(x,y,g);
endmodule

module carry(input wire p1,p0,g1,g0, output wire p, g);
    wire t;
    and2 a1(p1,p0,p);
    and2 a2(p1,g0,t);
    or2 o2(t,g1,g);
endmodule

module sum(input wire x, y, g, output wire s);

```

```

        xor3 x3(x,y,g,s);
endmodule

module prefixAdd(input wire [7:0]a,b, input wire cin, output wire [7:0] S);
    wire p[7:0],g[7:0];
    wire cp[7:0],cg[7:0];
    wire cp21,cg21,cp43,cg43,cp54,cg54,cp65,cg65,cp64,cg64;

    prop_gen p_0(a[0],b[0],p[0],g[0]);
    prop_gen p_1(a[1],b[1],p[1],g[1]);
    prop_gen p_2(a[2],b[2],p[2],g[2]);
    prop_gen p_3(a[3],b[3],p[3],g[3]);
    prop_gen p_4(a[4],b[4],p[4],g[4]);
    prop_gen p_5(a[5],b[5],p[5],g[5]);
    prop_gen p_6(a[6],b[6],p[6],g[6]);
    prop_gen p_7(a[7],b[7],p[7],g[7]);

    assign cp[0] = 1'b0;
    assign cg[0] = 1'b0;

    carry c1(p[0],1'b0,g[0],cin,cp[1],cg[1]);
    carry c3_0(p[2],p[1],g[2],g[1],cp21,cg21);
    carry c5_0(p[4],p[3],g[4],g[3],cp43,cg43);
    carry c7_0(p[6],p[5],g[6],g[5],cp65,cg65);

```

```

carry c2(p[1],cp[1],g[1],cg[1],cp[2],cg[2]);
carry c3_1(cp21,cp[1],cg21,cg[1],cp[3],cg[3]);
carry c6_0(p[5],cp43,g[5],cg43,cp54,cg54);
carry c7_1(cp65,cp43,cg65,cg43,cp64,cg64);

carry c4(p[3],cp[3],g[3],cg[3],cp[4],cg[4]);
carry c5_1(cp43,cp[3],cg43,cg[3],cp[5],cg[5]);
carry c6_1(cp54,cp[3],cg54,cg[3],cp[6],cg[6]);
carry c7_2(cp64,cp[3],cg64,cg[3],cp[7],cg[7]);

```

```

sum s0(a[0],b[0],cin,S[0]);
sum s1(a[1],b[1],cg[1],S[1]);
sum s2(a[2],b[2],cg[2],S[2]);
sum s3(a[3],b[3],cg[3],S[3]);
sum s4(a[4],b[4],cg[4],S[4]);
sum s5(a[5],b[5],cg[5],S[5]);
sum s6(a[6],b[6],cg[6],S[6]);
sum s7(a[7],b[7],cg[7],S[7]);

```

```
endmodule
```

TESTBENCH FILE CODE:

tb_prefix_add.v:

```
module tb_prefix;
```

```

reg [7:0] t_a,t_b;

reg t_cin;

wire [7:0] t_S;

initial begin $dumpfile("dump.vcd"); $dumpvars(0, tb_prefix); end

prefixAdd pra (.a(t_a), .b(t_b), .cin(t_cin), .S(t_S));

initial
begin

    t_a [7:0] = 8'b00000000; //0

    t_b [7:0] = 8'b01000001; //65

    t_cin = 1'b0;

    #5

    t_a [7:0] = 8'b01100100; //100

    t_b [7:0] = 8'b00011000; //24

    t_cin = 1'b0;

    #5

    t_a [7:0] = 8'b00010100; //20

    t_b [7:0] = 8'b10110010; //178

    t_cin = 1'b0;

    #5

    t_a [7:0] = 8'b00100001; //33

    t_b [7:0] = 8'b00111111; //63

    t_cin = 1'b0;

    #5

    t_a [7:0] = 8'b01100100; //100

    t_b [7:0] = 8'b00110010; //50

    t_cin = 1'b0;

```

```
#5  
t_a [7:0] = 8'b01100100; //100  
t_b [7:0] = 8'b00101000; //40  
t_cin = 1'b0;
```

```
#5  
t_a [7:0] = 8'b10110001; //177  
t_b [7:0] = 8'b00110110; //54  
t_cin = 1'b0;
```

```
#5  
t_a [7:0] = 8'b01011010; //90  
t_b [7:0] = 8'b00111100; //60  
t_cin = 1'b0;
```

```
#5  
t_a [7:0] = 8'b00011000; //24  
t_b [7:0] = 8'b01001100; //76  
t_cin = 1'b0;
```

```
#10  
t_a [7:0] = 8'b00000000;  
t_b [7:0] = 8'b00000001;  
t_cin = 1'b0;
```

```
end
```

```
endmodule
```


Output:

